

NATIONAL INSTITUTE OF TECHNOLOGY

AGARTALA, TRIPURA(WEST)



NAME - Arghajit Bhomik

ENROLLMENT NO - 20UCS134

REGISTRATION NO - 2012724

SUBJECT - DCLD LAB

BRANCH - Computer Science and Engineering

SECTION - B

1 EXPT NO. 4:

1.1 STUDY OF BOOLEAN EXPRESSION SIMPLIFICATION

Objective:

To study the Boolean rules & Boolean expression simplification Equipments:
Logic circuit simulator pro application

Theory

Here is the list of rules used for the Boolean expression simplifications.

- ***The Idempotent Laws:***

Idempotent Law states that combining a quantity with itself either by logical addition or logical multiplication will result in a logical sum or product that is the equivalent of the quantity.

$$A.A = A \quad A + A = A$$

- ***The Associative Laws:***

This law allows the removal of brackets from an expression and regrouping of the variables

$$(A.B).C = A.(B.C) \quad (A + B) + C = A + (B + C)$$

- ***The Commutative Laws:***

The order of application of two separate terms is not important.

$$A.B = B.A \quad A + B = B + A$$

- ***The Distributive Laws:***

This law permits the multiplying or factoring out of an expression.

$$A.(B + C) = A.B + A.C \quad A + B.C = (A + B).(A + C)$$

- ***The Identity Laws:***

A term OR'ed with a "0" or AND'ed with a "1" will always equal that term.

$$A.F = F \quad A.T = A \quad A + F = A \quad A + T = T$$

- ***The Complement Laws:***

A term AND'ed with its complement equals "0" and a term OR'ed with its complement equals "1".

$$A.A' = 0 \quad A + A' = 1$$

• **The Involution Law:**

$$A = A$$

De-Morgan's Law:

1. Two separate terms NOR'ed together is the same as the two terms inverted (Complement) and AND'ed for example $(AB)' = A' + B'$


2. Two separate terms NAND'ed together is the same as the two terms inverted (Complement) and OR'ed for example $(A + B)' = A'B'$

(T - True - 1 and F - False - 0)

2 Simplify: $C + (B.C)'$:

Expression	Rule(s) Used
$C + (B.C)'$	Original Expression.
$C + (B' + C')$	DeMorgan's Law.
$(C + C') + B'$	Commutative, Associative Laws.
$T + B'$	Complement Law.
T	Identity Law.

Fig-

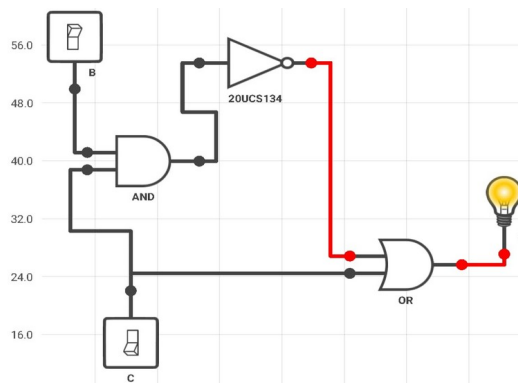


Expression	Rule(s) Used
------------	--------------

Rule(s) Used

Fig-

The diagram illustrates a logic circuit for a 2-bit adder. It consists of two 4-bit input registers, A and B, which provide inputs to a series of logic gates. The circuit includes NOT, AND, and OR gates. The outputs of these gates are connected to a 20UC5134 chip and a light bulb labeled 'Light 25'. The circuit is designed to perform a 2-bit addition of the values in registers A and B.

A' Complement. Identity.

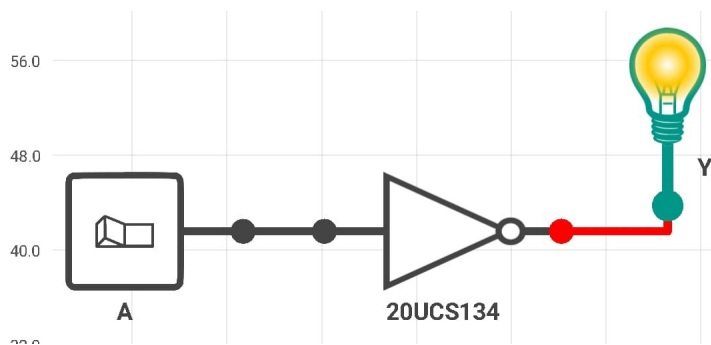


4 Simplify: $(A + C).(A.D + A.D') + A.C + C$:

1 Expression

Rule(s) Used

$(A + C).(A.D + A.D') + A.C + C$ Original Expression

Fig-

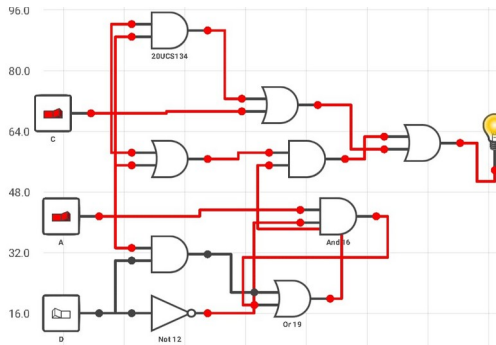

$(A + C).A.(D + D') + A.C + C$

Distributive.

$(A + C).A + A.C + C$

Complement, Identity.

$A((A + C) + C) + C$

Commutative. Distributive.

$A.(A + C) + C$

Associative. Idempotent

$A.A + A.C + C$

Distributive


$A + (A + T).C$

Idempotent, Identity, Distributive.

$A + C$

Identity, twice.

Fig-

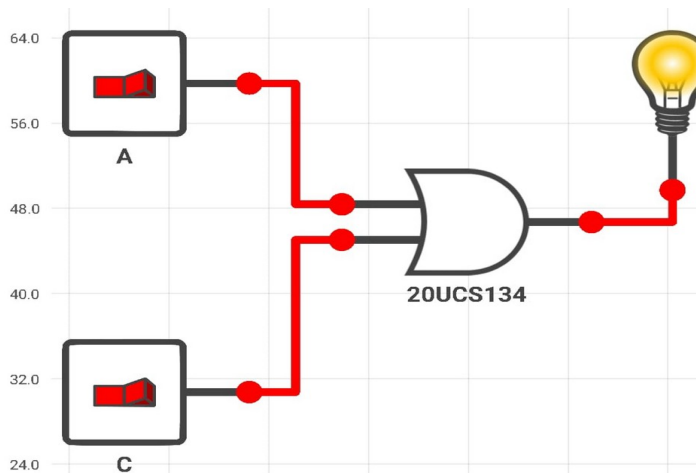

5 Simplify: $A.(A + B) + (B + A.A).(A + B')$:


Expression

Rule(s) Used

$A'.(A + B) + (B + A.A).(A + B')$

Original Expression

Fig-

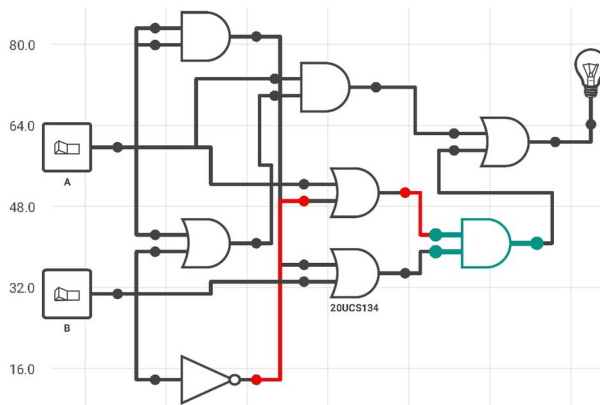

$A'.A + A'.B + (B + A).A + (B + A).B'$

Idempotent ($A.A$ to A),

$A'.B + (B + A).A + (B + A).B'$

Complement, then Identity.

$A'.B + B.A + A.A + B.B' + AB'$

Distributive, two places

$A'.B + B.A + A + AB'$

Idempotent (for the A's)

$A'.B + A.B + A.T + A.B'$

Commutative, Identity

$A'.B + A.(B + T + B')$

Distributive.

$A'.B + A$

Identity

$A + A'.B$


Commutative.

$(A + A').(A + B)$

Distributive.

$A + B$

Complement, Identity

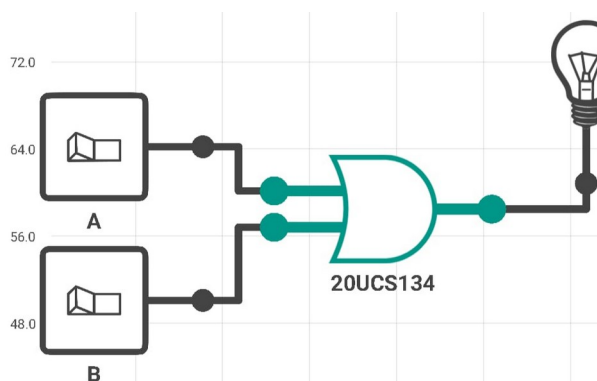


6 Simplify: $(A+B).(A+C)$

Expression

Rule(s) Used

$$A.A + A.C + A.B + B.C$$

Distributive law

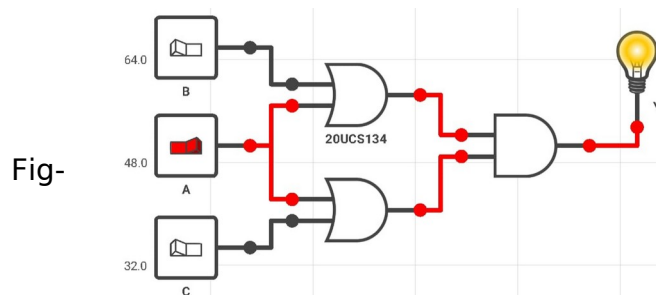

$$A + A.C + A.B + B.C$$

Idempotent AND law ($A.A = A$)

$$A.(1 + C) + A.B + B.C$$

Distributive law

$$A.1 + A.B + B.C$$

Identity OR law ($1+C = 1$)

$$A.(1 + B) + B.C$$


Distributive law

$$A.1 + B.C$$

Identity OR law ($1+ B = 1$)

$$A + (B.C)$$

Identity AND law ($A.1 = A$)

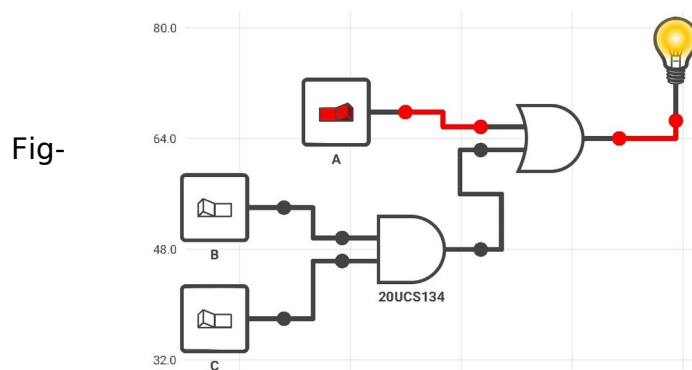


7 Simplify: $A.B + A.(B + C) + B.(B + C)$

Expression

Rule(s) Used

$A.B + A.B + A.C + B.B + B.C$ Distributive law

Fig-

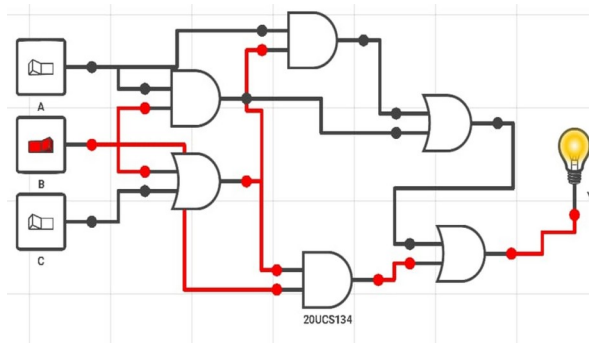

$A.B + A.B + A.C + B + B.C$ Idempotent law

$A.B + A.C + B + B.C$ Idempotent law

$A.B + A.C + B$ Absorption law

$B + A.C$ Absorption law

Fig-

